 


Learn Electronics	Projects	Reviews	High Voltage	Science	Microcontrollers	Vintage Electronics	Radio/Wireless
Ideas/Tips/Inspiration					Most Popular		



SERIES

The Arduino Graphics Interface

Turn an Arduino Due and a leftover analog oscilloscope into a high resolution computer graphics display

Don't Miss Out!

Get our FREE Cool Reads newsletter and feed your brain with great electronics projects, tutorials, and other specially selected content. Delivered right to your inbox 4 times per month!

X

THE ARDUINO GRAPHICS INTERFACE – PART 1

By [Edward Andrews](#) [View In Digital Edition](#)

[» Skip to the Extras](#)

DESIGN CONCEPTS AND HARDWARE FABRICATION

The early days of electronic computers used teletype machines and line printers, and later, alphanumeric screens and keyboards as their primary input-output devices. As computer usage grew beyond census and accounting applications, the need for improved graphical displays and output devices became apparent.

Graphical display terminals using large screen cathode ray tubes (CRT) soon evolved. These displays were essentially “up-sized oscilloscopes” whose X-Y beam deflection was driven by a computer.

Figure 1 shows a specialized XY CRT terminal that was part of SAGE (Semi-Automatic Ground Environment): an early air defense system deployed in the US.



Get It Now!

- ALL ARTICLES IN THIS SERIES:
- [Part 1 – Design Concepts and Hardware Fabrication](#)
 - [Part 2 – Software Concepts and Support Library](#)

LATEST NEWSLETTERS

MARCH 12, 2021

[Wirespondence, Serial Bluetooth with a Micro, Analog Front End, AM/FM Receiver Restoration](#)

- [Wirespondence!](#)
- [Using Serial Bluetooth With a Microcontroller](#)
- [Why You Need an Analog Front End and How to Set It Up](#)
- [Restoring a Vintage Zenith Table Top AM/FM Receiver from the '60s](#)

MARCH 05, 2021

FIGURE 1. SAGE air defense system used an XY interactive graphics terminal.

By the late '70s, Tektronix, Hewlett-Packard, and others sold general-purpose XY graphics terminals able to show graphs, charts, and line drawings of all types.

While a far cry from what we take for granted today, these were important stepping-stones in the evolution of computer graphics and display technology.

ARDUINO GRAPHICS INTERFACE

As an undergrad electrical engineering student some eons ago, I worked on a MODCOMP (Modular Computer Systems, Inc.) 16-bit minicomputer that featured a large 19" Hewlett-Packard XY graphics display screen. A few months ago, I began to wonder: *Would it be possible to replace those half dozen racks of circa 1975 minicomputer hardware with one of today's \$50 credit-card sized computers?*

The answer proved to be YES! What resulted, I call the **Arduino Graphics Interface**, or **AGI** for short. With AGI, you can transform a leftover analog oscilloscope into a high resolution computer graphics display and gain valuable insights into computer graphics, digital-to-analog conversion (ADC), and advanced Direct Memory Access (DMA) hardware and software techniques. It's easy to add a real time clock (RTC) module and interactive controls to turn the AGI platform into a "CRT CLOCK" (**Figure 2**) or other resolution computer graphics display device.



FIGURE 2. AGI can become a CRT CLOCK!

In this article, we'll focus on the overall concepts, circuit design, and hardware fabrication. In Part 2, we'll integrate the hardware to **XYscope**: the software control and plotting library that enables an Arduino Due CPU + analog oscilloscope to become a high resolution XY graphics display. *Let's get started!*

AGI BLOCK DIAGRAM & OPERATIONAL OVERVIEW

The block diagram of the AGI is shown in **Figure 3**.

[Analog Waves from Digital Signals, DIY Electric Scooter, The Solar Alternative, Driving LEDs with a Microcontroller](#)

[Generating Analog Waves From Digital Signals](#)

[Build a DIY Electric Scooter](#)

[The Solar Alternative](#)

[Driving LEDs with a Microcontroller](#)

[VIEW ALL >](#)

Don't Miss Out!

Get our FREE Cool Reads newsletter and feed your brain with great electronics projects, tutorials, and other specially selected content. Delivered right to your inbox 4 times per month!

Get It Now!

[Stepper Motor Overview](#)

[Winding Single-Layer Air Coils](#)

[Wide-Range Current Regulator](#)

[Sawtooth Generator](#)

POPULAR STORIES

[Wirespionage!](#)

[RADAR And Electronic Warfare Fundamentals](#)

[Wire Wrap Is Alive And Well!](#)

[Turing Machines](#)

[1920s Radio Applause Cards](#)

LEARNING ELECTRONICS

Need to brush up on your electronics principles? These multi-part series may be just what you need!

[Understanding Digital Logic ICs](#)

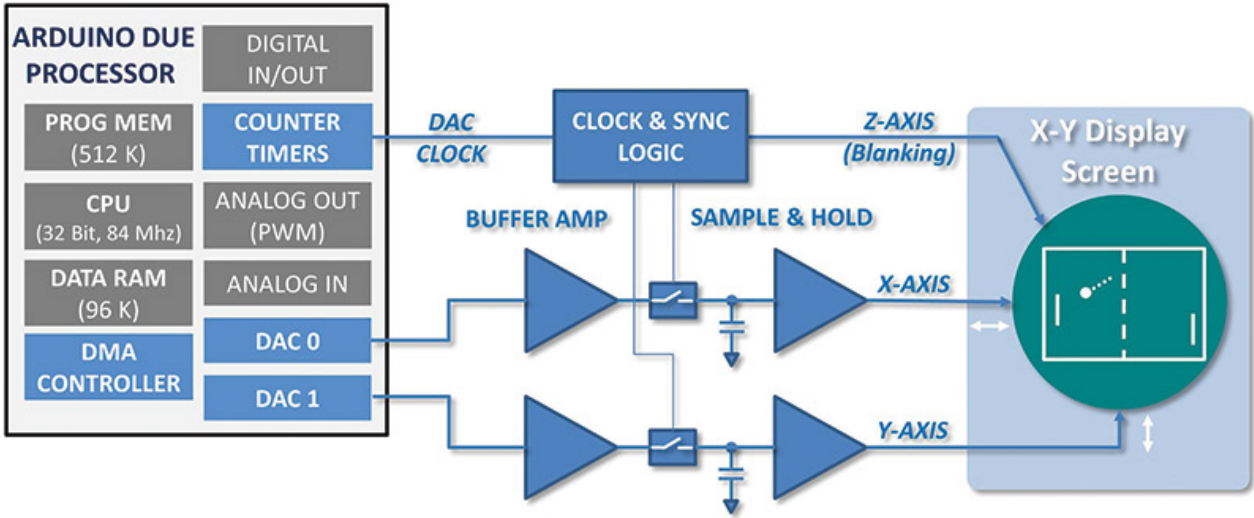


FIGURE 3. Arduino Graphics Interface block diagram.

You can see that a pair of digital-to-analog converters (DACs) inside of the ATMEEL SAM 32-bit CPU (the heart of an Arduino Due) is used to drive the X and Y axes of an analog oscilloscope. Rather than use the normal oscilloscope Amplitude vs. Time display mode, we run the scope in X-Y mode. That is, the internal oscilloscope time base that usually drives the X axis is *not used*, but rather all XY information for deflecting the CRT beam comes directly from the Arduino through the AGI circuits.

To create graphical images with AGI, the programmer need only build a list of 12-bit integers that make up the individual points we want to show. One after the other, the DACs of the Due receive and convert each XY integer coordinate pair into small X-Y voltages that drive the CRT beam about the oscilloscope screen. The block diagram shows that we also provide a blanking pulse (a.k.a., Z axis blanking) as a third signal to the scope.

As with all CRT type displays, one must repeatedly send the whole display list to the screen to keep the points visible and refreshed. Even though the points are actually flashing at a very high rate, human Persistence Of Vision (POV) causes the displayed image to appear stable and flicker-free.

KEY AGI FEATURES

- High Resolution** — By using 12-bit DACs, we have a display resolution of 4096 x 4096. This *exceeds* even HD TVs and beautifully renders smooth step-free lines, arcs, and characters.
- Easy to Use** — To display graphical images, the AGI programmer simply creates a list of XY integers to define the individual points to be plotted. A small background process automatically sends the point-list to the CRT.
- Ready to Use** — A graphics and control library of simple subroutine calls makes it easy to create and load graphic and alphanumeric content into the XY point-buffer. The AGI Library includes:

- Plot POINT, LINE, RECTANGLE, CIRCLE, ELLIPSE, CIRCLE-ARC-SEGMENT, ELLIPSE-ARC-SEGMENT
- Plot CHARACTER, TEXT_STRINGS, INTEGER NUMBERS, FLOATING POINT NUMBERS

- Complex Graphics Possible** — The display list can contain up to 15,000 X-Y points so that complex objects can be rendered.
- Fast** — The Due is a very fast processor that can very quickly calculate and store points into the XY display list array. There's plenty of processor time available to make changes in the list, making animated graphics easy.
- Educational** — The AGI is a great introduction to graphical coordinate systems, X-Y point/vector style computer graphics, and DACs.

AGI is also a solid demonstration platform to learn and utilize counter-timers and DMA technology.

- [Bipolar Transistor Cookbook](#)
- [Op-Amp Cookbook](#)
- [FET Principles And Circuits](#)
- [Triac Principles And Circuits](#)
- [Understanding Digital Buffer, Gate And Logic IC Circuits](#)
- [Smiley's Workshop: AVR C Programming Workshop](#)
- [Smiley's Workshop: Serial Communications Between An Arduino And A PC](#)
- [Checking Inductors](#)

Don't Miss Out!

Get our FREE Cool Reads newsletter and feed your brain with great electronics projects, tutorials, and other specially selected content. Delivered right to your inbox 4 times per month!

Get It Now!

- [Displays](#)
- [Signal Generators](#)

ARCHIVES

- [April 2017](#)
- [March 2017](#)
- [January 2017](#)
- [October 2016](#)
- [June 2016](#)
- [View complete archives list](#)

RECENT POSTS

- April 13 - [A Night at the Opera?](#)
- April 13 - [3D Printable Tractor Beam](#)
- March 07 - [Video Games Turn 50](#)
- March 07 - [Make Your Raspberries Touchable](#)
- January 27 - [World's Smallest Transistor — Sort of](#)

WHILE IT'S PRETTY COOL, THERE ARE SOME LIMITATIONS

The AGI uses an analog oscilloscope for its graphics output display. You'll have to dust off your old analog oscilloscope or perhaps buy a vintage unit off eBay. The Oscilloscope Requirements sidebar details the features you need to look for when evaluating possible scope candidates for use with this project. Since we use an oscilloscope as the display screen, the size and display color is fixed by the cathode ray tube inside the scope.

While each individual point is displayed on the screen as either 'full ON' or 'full OFF,' variable brightness is easily achieved by varying the point-density of the dots that make up each graphic feature (*more on this in Part 2*).

WHY AN ARDUINO DUE?

At first, I labored over the multitude of CPU boards available, but it soon became apparent only one board would "Due." (I know, it's a terrible pun.) Even though the Beagle Bone and Raspberry Pi families have faster CPUs and more memory, only the Arduino Due CPU includes a pair of DMA-driven on-chip DACs.

GETTING XY DATA OUT TO THE SCOPE

While programmed I/O using an Arduino *analogWrite()* command is a common way to output data to the DACs, the AGI uses DMA techniques. We'll discuss this further in Part 2, but for now, suffice it to say that we connect the DMA hardware inside the Due to a COUNTER-TIMER which automatically sends the X-Y data array out through the DACs to the oscilloscope screen at very high speeds.

DAC PERFORMANCE

For the AGI project, the Due provides two DAC outputs; each of which translates a 12-bit unsigned integer into one of 4,096 different analog voltage levels. As measured at the processor DAC pins, the CPU outputs a voltage of 0.5V when converting the integer value 0, and outputs 2.75V when converting the integer value 4095. Dividing this 2.25 volt peak-to-peak voltage range by 4096 means that each step or bit change at the DAC input results in a 550 μ V change at the DAC output. These signals are buffered by the AGI circuits before they are sent on to the oscilloscope for display.

In addition to resolution, DAC speed is also important. Speed is defined as the time it takes for the DAC to change its output voltage in response to a change at its digital input. A perfect DAC would have zero conversion time, but reality falls short. The rise times, fall times, and settling times of the DACs are important to the AGI project as they define the rate that can be used to send points to the scope screen; this, in turn, sets the maximum number of points we can display within our target POV window of 20 ms.

Since DAC speed is not specified in the ATMEL SAM datasheet, I wrote a small AGI program to drive the DACs from 0 to 4095 and then back to 0, so that I could make my own "worst case" full-scale speed measurements.

Using an oscilloscope to monitor the DAC outputs, **Figure 4** shows that a full-scale change in output of the DAC from 0 to 4095 in one step takes slightly over 300 ns. Similarly, the step going from 4095 back to 0 is seen to be about 300 ns as well.

RECENT COMMENTS

- [kadasddd](#)

Lol its actually useful

[Visual Hexadecimal](#) · [1 day ago](#)

- [Jenny Everywhere](#)

I did this months ago, using a "Beetle" 32u4 module with built-in USB plug, a buzzer for sidetone, a button for mode selection, and a socket for a key plug. It works with a straight key directly,...

[Can't Keyboard? Use Morse Code Instead](#) · [2 days ago](#)

- [Chris in Santa Cruz](#)

Nice article and a good discussion. I wish it was done on the widely used Arduino platform however. 73, Chris

[Can't Keyboard? Use Morse Code Instead](#) · [2 days ago](#)

- [David Goodsell](#)

Glad to hear that you hopefully had some good memories about your Erector set. Frankly I think society is sometimes a little too cautious about growing up. There were always risks. In my opinion it...

[The Magic of the Gilbert Erector Set](#) · [3 days ago](#)

- [yu tube](#)

Wow that brings back memories...it would keep me occupied (and out of mom and dad's hair) for hours every

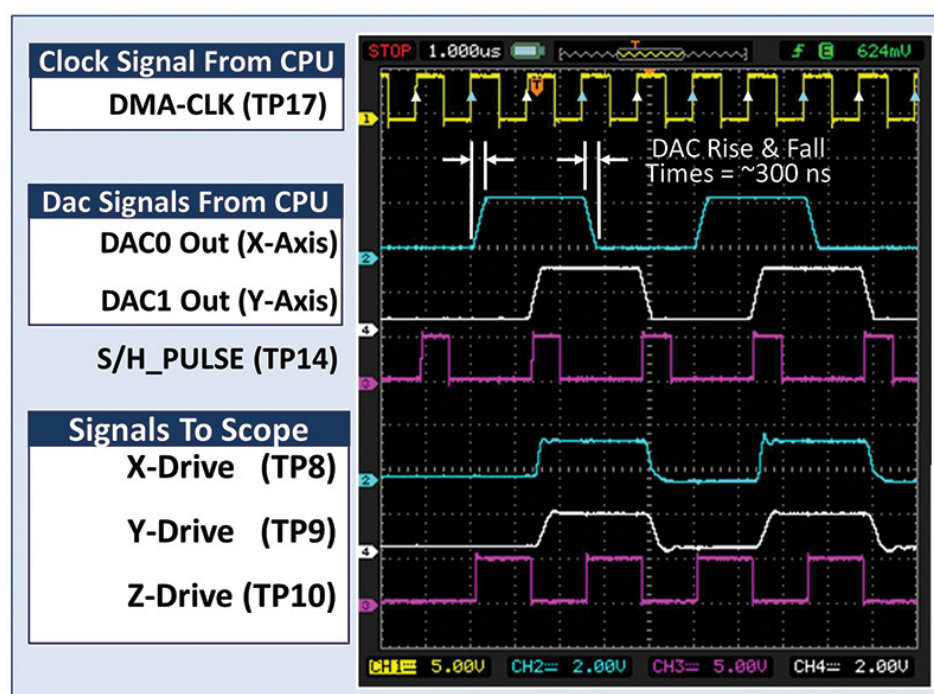


FIGURE 4. DAC speed and AGI timing signals.

Figure 4 also shows a few other aspects of the overall timing. First off, observe that the *DMA_CLK (TP17)* signal (one of the Due Counter-Timers) drives the rate of the DMA transfers and therefore the pace of digital-to-analog conversions.

Next, note that the X and Y conversions follow each other in time, with the DAC0 signal (the X axis value) changing first, followed one *DMA_CLK* cycle later by the DAC1 signal (Y axis). Analog sample and hold circuits are used to time-synchronize the X and Y signals to one another before they are sent out to the oscilloscope as the *X-Drive (TP8)* and *Y-Drive (TP9)* signals for display.

Finally, the Z axis signal *Z-Drive (TP10)* is used to turn the CRT Spot on (logic 1 = “unblank”) every time a new point pair is ready for display on the screen. The CRT Spot is then turned off (logic 0 = “blanked”) just before the X-Y signals are “moved” to the next point to be plotted. Blanking the beam in this way keeps the display crisp and free of DAC settling times and other point-to-point transition artifacts.

Given the DAC rise and fall times, it’s possible to determine the highest *DMA_CLK* frequency we can use. My tests show reliable high quality graphics plotting can be achieved at *DMA_CLK* frequencies up to 800 kHz. Above 800 kHz, the DAC rise and fall time delays begin to distort the graphics display, appearing as incorrectly plotted points on the oscilloscope screen whenever adjacent members in the XY list are far away from one another.

USING A TIMER TO TRIGGER CRT REFRESH

As noted, we need to repeat the DMA transfer over and over again to keep the CRT scope screen lit up. To do this, the AGI uses a second timer to create a “Time-to-Refresh” interrupt once every 20 ms. Every time we receive this interrupt, a new CRT screen-paint cycle is initiated. This repaints the screen 50 times per second, above discernable POV flicker rates.

With the *DMA_CLK* frequency set to 800 kHz, it’s possible to send about 10,000 points to the screen within the 20 ms target refresh interval. When more than 10K points are present in the display list, the software driver will automatically extend the refresh interval as needed so all points can be displayed. Depending on the phosphor decay characteristics of your oscilloscope screen and your personal POV sensitivity, you will probably notice the onset of image flicker when plotting more than about 12,000 points.

CIRCUIT DETAILS AND THEORY OF OPERATION

day. and it came with hundreds of easy to swallow small pieces and chocking hazards for my...

[The Magic of the Gilbert Erector Set · 3 days ago](#)

The AGI schematic is shown shortly in **Figures 7-9**. I've included many test points (**TPxx**) in the design to facilitate testing and troubleshooting.

POWER SUPPLY — Any wall wart that can supply 12-15 VDC at .5 amps can be used to power the AGI circuitry. As shown in **Figure 5**, onboard linear regulators provide clean low-noise regulated +9.75V and +5.0V outputs to power both the AGI analog circuits (9.75V) as well as the logic and Arduino Due CPU (5.0V).

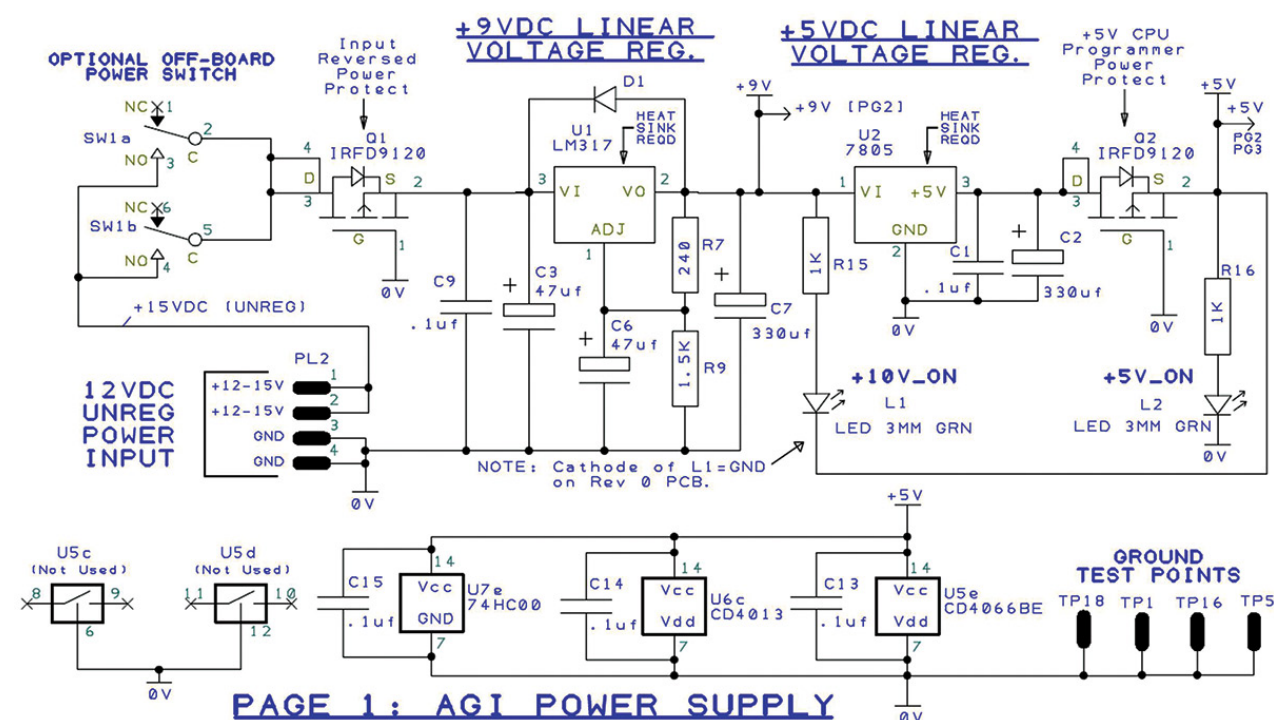


FIGURE 5. AGI power supply circuits.

Construction Note: Both voltage regulators U1 and U2 get warm and must be mounted to heatsinks. The two devices must use insulating hardware if they share a common heatsink or if either heatsink is grounded. Use large heatsinks to dissipate more heat if driving the AGI power input with more than about 12 VDC.

X-Y BUFFER AMPS — In **Figure 6**, you can see that the DAC0 (X axis) and DAC1 (Y axis) signals from the Due are received and buffered by high frequency op-amp U4. Potentiometers are provided at this stage so that signal gain (amplitude) and offset (screen position) for X and Y can be independently set. The gain pot on each output will vary the amplitude within a 1.0V to 4.0V P-P range. The centering pot varies the signal offset so that it can reside anywhere within a .2V to 4.75V window. Final display adjustment will be a combination of these AGI pots, as well as the oscilloscope gain and centering controls; my scope works well with AGI outputs adjusted to 1.5V P-P centered about +2.5 VDC.

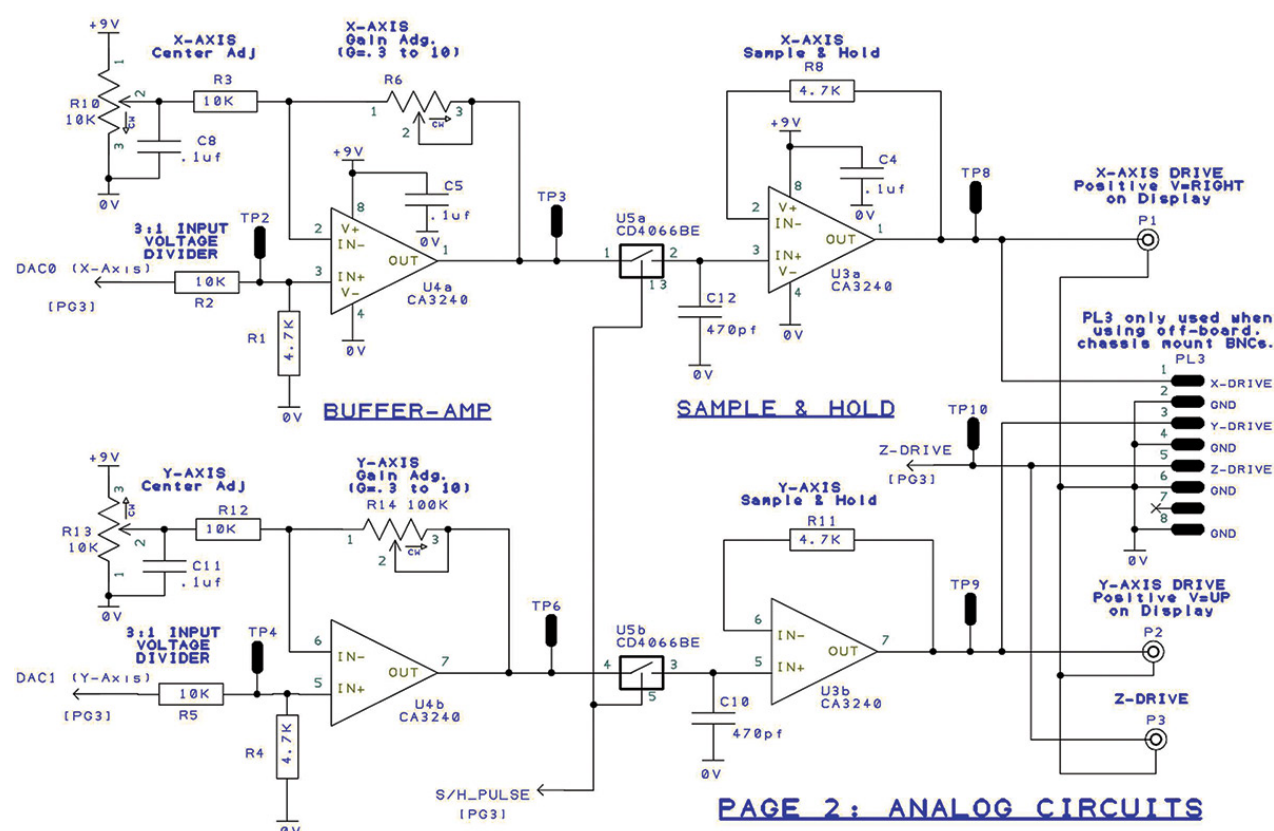


FIGURE 6. Analog section of AGI circuitry.

SAMPLE AND HOLD CIRCUITS — As seen in **Figure 4**, the DAC0 and DAC1 outputs are not simultaneously output by the Due CPU; the X value is converted first, followed by the Y value one *DMA_CLK* cycle later. Analog switch U5a-b, hold capacitors C9 and C13, and buffer amps U3a-b make up the pair of Sample and Hold (S/H) circuits that align and synchronize the X-Y point pair voltages, so they change together when they're sent to the oscilloscope for display. The X and Y buffer amps are followed by transmission gates U5a-b and output op-amps U7a-b which work together to form two independent S/H circuits.

So, how do these S/H circuits work? Looking at the X axis path, it shows that whenever transmission gate U5a is turned on, the X axis voltage output of U4a is connected to C12 and buffer amp U3a. When U5a is turned off, C12 stores (a.k.a., “remembers”) the voltage, holding the X axis voltage stable even though the DAC output itself begins to change in response to the next conversion cycle.

U5b, C10, and U3b perform the same S/H function for the Y axis signal.

DATA CLOCK TIMING — *COUNTER_TIMER_0* of the Due is programmed to be the *DMA_CLK*. This signal drives the internal DMA operations, but as shown in **Figure 7**, also comes to the outside world through CPU pin D2. This signal is fed to U6a and U8b to create all the needed AGI timing signals. Flip-flop U6a divides the *DMA_CLK* by 2 to create a signal that represents a *point pair transfer completed* signal or *POINT_CLK*. The *POINT_CLK_NOT* signal is then combined to generate the *S/H_PULSE* and the *SHOW_POINT* signals. As depicted in the timing traces of **Figure 4**, the *S/H_PULSE* signal is used to “grab and hold” the X-Y voltage pair. Then, the *SHOW_POINT* pulse is sent to the Z axis of the oscilloscope (a.k.a., “Z-Drive”) to unblank each point after it has settled down and is ready to be illuminated.

PAGE 3: DATA CLOCK TIMING & BLANKING

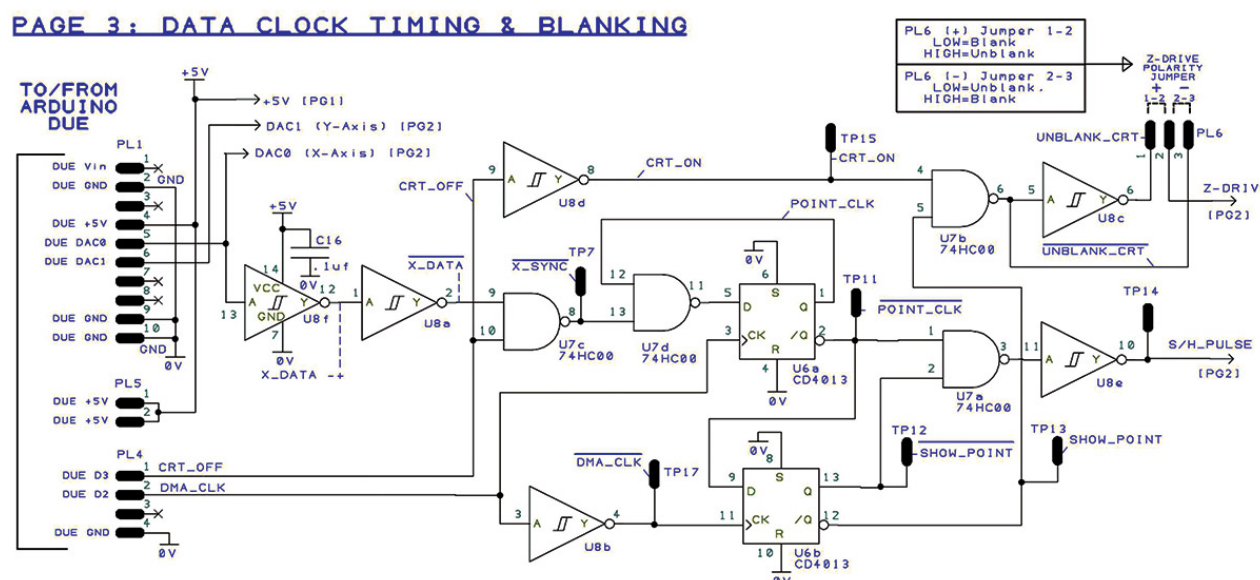


FIGURE 7. Timing and logic.

Build Note: Jumper PL6 is used to select the “blanking polarity” and is set to match the blanking logic used by our particular oscilloscope.

BLANKING SYNCHRONIZATION — It might seem a bit unusual to see the analog output of DAC0 (X axis) also connected and as a *digital input* to gate U8f. While this looks a little weird, it's a vital part of the X-Y axis signal synchronizing process.

You see, the AGI circuitry needs to synchronize the *S/H_PULSE* and *SHOW_POINT* signals to the actual *XY_list* data being sent out of the DACs. To do this, the AGI software routine *XYscope.plotStart()* loads a defined full-scale pulse pattern into the first few locations of the *XY_List* array, immediately ahead of the actual points generated by the application code for display. This synchronizing pulse signal comes through the DAC0 port and is detected by U8f, inverted by U8a, and then combined with *CRT_OFF* (gate U7c) to become the *X_SYNC_NOT* signal.

In conjunction with gate U7d and flip-flop U6a, a perfectly synchronized *POINT_CLK_NOT* is created that is used to then generate the *SHOW_POINT* and the *S/H_PULSE* signals.

You also see another signal coming from the Due on digital output port D3 called *CRT_OFF*. When D3 is set to TRUE (logic 1), the CRT beam is forced off no matter what the other signals are doing. When D3 is set to FALSE (logic 0), the CRT beam is ENABLED to flash on for every point plotted to the screen. The AGI control code drives this signal pin to the *CRT_ON* state at the start of every refresh cycle, and then drives the pin to the *CRT_OFF* state at the end of every refresh cycle. To prevent CRT image burn, this signal is also set to *CRT_OFF* when the software screen saver routine built into the AGI software times out.

A FEW GUIDELINES AND CAUTIONS

Due LOGIC VOLTAGE LEVELS — We are constantly reminded not to mix 5V and 3V logic! At first glance, it appears that I have broken this rule since some 3.3V Due outputs *are directly connected* to a few AGI 5V logic gate inputs. What's up with that? Actually, it's okay to connect 3V *outputs* to 5V logic *inputs*; 5V logic devices will properly interpret 3V logic levels. This type of direct connection is allowed, *but only as long as there are NO pull-up resistors to +5V*.

USE CAUTION: *NEVER EVER connect external 5V logic outputs directly to Due logic inputs*; doing so will over-voltage the input circuits and permanently damage the CPU chip.

ANALOG OUTPUT LOADING — In pouring through the Internet for background information, I saw numerous concerns and problems connecting to and using the DAC0 and DAC1 pins of the Due. It turns out that when configured as analog DAC outputs, these pins have limited analog drive and minimal short circuit protection. This means that even a momentary short to ground or power will 'fry' the DAC output pins. Unfortunately, I can confirm this sensitivity! **USE CAUTION:** *DAC outputs should only be connected to high impedance (>2K ohm) loads and never shorted to POWER or GROUND*. Use **extreme care** when placing scope probes on or off the CPU DAC pins.

BUILDING THE AGI

You can't go wrong purchasing an authentic Arduino Due board for this project from www.arduino.cc (about \$50 each). However, since the Due design is open source, Due-compatible boards are also available from several other places. Once you have the Due in hand, the AGI interface circuit must be built. I prototyped the AGI circuit using a solderless breadboard (**Figure 8**) and later built a more robust point-to-point soldered-wire version.

 


FIGURE 8. My first breadboard prototype.

An extensive AGI **Parts List** and detailed build and test document can be found with the article downloads. While the **Parts List** shows Digi-Key part numbers, nothing is exotic, and most of the parts can be sourced from nearly any distributor or surplus channel.

Feel free to substitute alternate parts as needed to utilize your “on-hand stock room.” However, I will add that it did take me a while to get the CA3020 op-amps to behave well running off of a single power supply. If you do substitute the op-amps, be sure to choose alternates that can run from a single power supply while also having stable high frequency (>3 MHz) performance. Slow audio-grade op-amps such as the LM392 will not work.

Once the circuit design was solid, I used Design Spark PCB V8.0 to create a small two-layer PCB (printed circuit board) for the AGI project. Design Spark is a well featured circuit board package that is available free from RS Components. Like all PCB software, Design Spark has a bit of a learning curve.

While it may not be the best choice for someone new to PCB layout, once you understand how “it thinks,” DESIGN SPARK performs quite well.

The completed AGI PCB is seen in **Figure 9**.

 


FIGURE 9. AGI circuit board.

Since I wanted to keep things simple and easy to build, I opted to use only through-hole components for this project. I made the AGI PCB a little larger than a standard Arduino board so that the Due could be easily mounted on top of the AGI circuit board using 4-40 spacers.

Figure 10 shows that the connections between the AGI and the Due are easily accomplished with just a few wires.

 


FIGURE 10. Connecting the AGI to the Due.

With this scheme, you remain free to add any shield board that you might need atop the Due. I found the PCB version of the AGI provided a huge performance improvement over my earlier hand-wired builds.

The large bottom layer ground plane on the PCB greatly reduced the noise sneaking into the analog circuits which improved overall image quality. You will find a complete set of Gerber PCB files with the downloads so that you can have PCBs made by your favorite circuit board fab house.

COMING UP IN PART 2: GETTING GOING WITH THE AGI SOFTWARE

Just like any other Arduino project, the AGI system can be programmed using the Arduino Integrated Development Environment (IDE). In Part 2, we'll focus on the software by looking at *CRT_SCOPE*: a test and checkout program that you can use to get your build up and running. We'll also use this program as a vehicle to demonstrate how easy it is to use XYscope: the Arduino AGI software support library.

You can get ready for Part 2 by downloading and installing the Arduino IDE, Due board definition files, Due timer library, and the AGI library. If this is your first Arduino Due project, I suggest you start out with some basic “hello world” and “blinking LED” test programs to get the IDE set up, compiling, and properly connected to your Due. Check out the References for links to the IDE and a few others that you might find interesting.

See you next time! **NV**

[The Arduino Graphics Interface - Part 2](#)

Get The PCB and *Start Experimenting!*


AGI OSCILLOSCOPE REQUIREMENTS

Overall plot quality is influenced by the quality and performance of the oscilloscope and CRT used. This project works well only with *analog* oscilloscopes; digital scopes will only produce poor looking output.

There are many analog scopes manufactured by Tektronix, HP, Phillips, Leader, GW-Instek, and others that will work well. Used models are often available starting at less than \$50. Look for these key features as you evaluate scope candidates:

- Screen size: Larger is better!
- For best display quality, scope frequency response should be 10 MHz or more.
- Scope must support an X-Y operating mode.

 — Scopes that support XY mode typically have panel markings that clearly show XY inputs and settings.



- Scope must have a Z axis or “Intensity Drive” input.
- Check the rear panel of the scope to find this feature.



PARTS LIST

ITEM #	REF DESIGNATORS	QTY	VALUE/NOTES	PACKAGE
1	C10, C12	2	470 pf	DSC
2	C11, C13, C14, C15, C16, C4, C5, C8, C9	9	.1 µF	DSC
3	C2, C7	2	330 µF	DSCV
4	C3, C6	2	47 µF	DSCV
5	D1	1	1N4004	DIOD05
6	L1, L2	2	LED 3 MM GRN	DSC
7	P1, P2, P3	3	Can use chassis mnt BNC	USER
8	PL1	1	Can use soldered wire	SIP
9	PL2	1	Can use soldered wire or alternate connector	DSC
10	PL3	1	Can use soldered wire	SIP
11	PL4	1	Can use jumper wire	DSC

12	PL5	1	Can use soldered wire	DSC
13	PL6	1	Can use jumper wire	DSC
14	Q1, Q2	2	IRFD9120	DIL
15	R1, R11, R4, R8	4	4.7K	DSC
16	R10, R13	2	10K	USER
17	R12, R2, R3, R5	4	10K	DSC
18	R14, R6	2	100K	USER
19	R15, R16	2	1K	DSC
20	R7	1	220	DSC
21	R9	1	1.5K	DSC
22	SW1	1		USER
23	TP1, TP10, TP11, TP12, TP13, TP14, TP15, TP16, TP17, TP18, TP2, TP3, TP4, TP5, TP6, TP7, TP8, TP9	18	OPTIONAL	DSC
24	U1	1	LM317	DSC
25	U2	1	LM7805	DSC
26	U3, U4	2	CA3240	DIL
27	U5	1	CD4066	DSC
28	U6	1	CD1013BE	DSC
29	U7	1	74HC00	DIL
30	U8	1	74LS14	DIL
31	PC1	1	20180805R0	2-LAYER
32	CBL1	3	BNC CBL TO SCOPE (builder supplied)	CBL

DOWNLOADS

 [download](#)

201802-Andrews.zip

What’s in the zip?

BOM
Build Doc

Share 38 Like Be the first of your friends to like this.

COMMENTS

10 Comments

Nuts & Volts

 Disqus' Privacy Policy


 Login

 Recommend 2

 Tweet

 Share


Sort by Best




Join the discussion...

LOG IN WITH

OR SIGN UP WITH DISQUS






Name


 **Steve Selby** • 20 days ago • edited

Forget the Gerbers, the whole PCB is actually unnecessary. The Arduino Due is quite capable of driving an XY display without any added hardware. Furthermore, the Z channel isn't needed either which helps because many scopes don't have a Z input. Check out this video to find out more.



Arduino Due Vector Graphics Display




 |  • Reply • Share ›

 **papa smurf** • a year ago



Where are the Gerbers? There are none in the download and I would like to fab a PCB. Thanks.


 |  • Reply • Share ›

 **nutsvolts** → papa smurf • a year ago • edited



Here's a direct link to Ed's github page with all kinds of details:
<https://github.com/Ed-EE-En...>


This link is provided at the end of Part 2 as well.

 |  • Reply • Share ›



 **nutsvolts** → nutsvolts • a year ago


<https://github.com/Ed-EE-En...>

 |  • Reply • Share ›



 **RobertoAguilarPerez** • 2 years ago

I like to buy a totally functional device for use as a subsystem on another project. Can you help me?
radioservicioaguilar@hotmail.com

 |  • Reply • Share ›

 **finnich** • 3 years ago

Added to the recommendation...Loved the way it is deeply explained...I am building it right now!


 |  • Reply • Share ›

 **Henk Gooijen** • 3 years ago


Excellent article, great job, very nice!

Is anybody going to make a batch of the PCB?


is anybody going to make a batch of the PCB?
I would love to buy a PCB (I'm in The Netherlands).
^ | v • Reply • Share ›

 **Vern Graner** ➔ Henk Gooijen • 3 years ago


Hi Henk! There is a PCB available for this kit in the Nuts and Volts store here:
<https://store.nutsvolts.com...>
Hope that helps! :)
^ | v • Reply • Share ›

 **Henk Gooijen** ➔ Vern Graner • 2 years ago

Hi Vern,
I should be ashamed ... one year elapsed so fast!
But I do have the PCB, all components are soldered. Next step is
programming the Arduino ... soon ...
^ | v • Reply • Share ›

 **Tacheon** • 3 years ago

 Amazing documentation! I'm gathering parts now and I plan to drive the CRT tube
with HV XYZ circuitry.



2020 ISSUE-3

.....
[How You Can Intercept Secret Messages Being Sent to Spies](#)
.....
[Transformer Based Power for Nixies](#)
.....
[Oscillators, Statistics, Q, and Muons](#)




2020 ISSUE-2

.....
[Restoration of a Vintage Telefunken Jubilate 5161W AM/SW/FM Receiver](#)
.....
[Build a DIY Electric Scooter](#)
.....
[Build an Automatic Card Shuffler](#)



2020 ISSUE-1

 .....
[Remembering the Crystal Radio](#)
.....
[Build an AM Transmitter for Use with Antique Radios](#)
.....
[An Introduction to the Parallax Propeller 2](#)



2019 ISSUE-6

.....
[Copper Cobweb Circuit Construction](#)
.....
[A Real-Time Operating System for the Arduino](#)
.....
[Build a Castle in the Clouds](#)

CONNECT WITH US



SUBSCRIBE TO OUR NEWSLETTER

Sign Up Now